

University of California
Berkeley
College of Engineering
Department of Electrical Engineering
and Computer Science


Robert W. Brodersen
EECS140

Analog Circuit Design

**Lectures
on
STABILITY**


Effect of Feedback on Frequency Response

SB-1

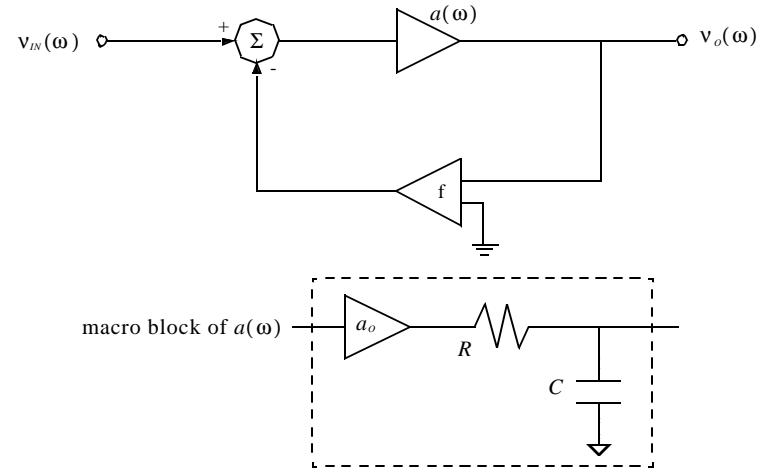

Effect of Feedback on Frequency Response (Cont.)

SB-2

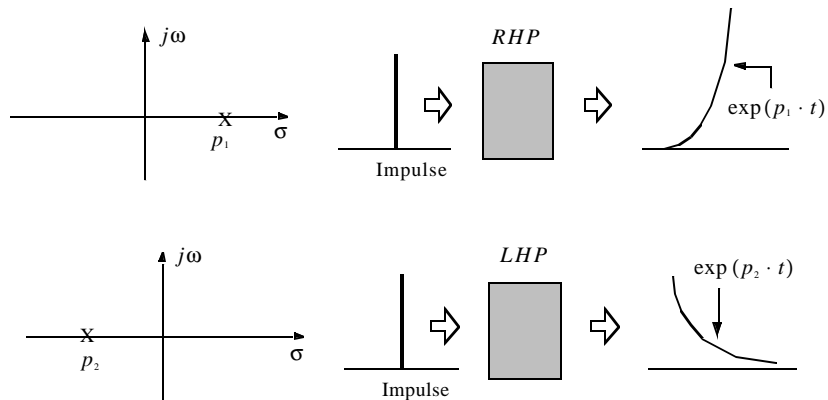

Effect of Feedback on Frequency Response (Cont.)

SB-3

Let $a(\omega)$ be a single pole response,

$$a(s) = \frac{a_o}{1 - \frac{s}{p_1}} \Leftrightarrow a(\omega) = \frac{a_o}{1 + j \frac{\omega}{\omega_{p1}}}$$

$$p_1 = -\omega_{p1}$$

$$\frac{v_{out}(s)}{v_{in}(s)} = A(s) = \frac{a(s)}{1 + a(s) \cdot f} = \frac{1}{f} \left(\frac{T(s)}{1 + T(s)} \right)$$


$$A(s) = \frac{\frac{a_o}{1 - \frac{s}{p_1}}}{1 + \frac{a_o}{1 - \frac{s}{p_1}} \cdot f} = \frac{a_o}{1 + a_o \cdot f} \left(\frac{1}{1 - \frac{s}{p_1 \cdot (1 + a_o \cdot f)}} \right)$$

Effect of Feedback on Frequency Response (Cont.) SB-4

Let $T_o = a_o \cdot f$


$$A(s) = \frac{a_o}{1 + T_o} \cdot \left(\frac{1}{1 - \frac{s}{p_1 \cdot (1 + T_o)}} \right)$$

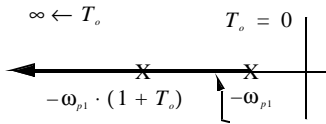Pole is at $p_1 \cdot (1 + T_o) \Rightarrow -\omega_{p1} \cdot (1 + T_o)$



Root Locus - motion of poles as loop Gain is increased.

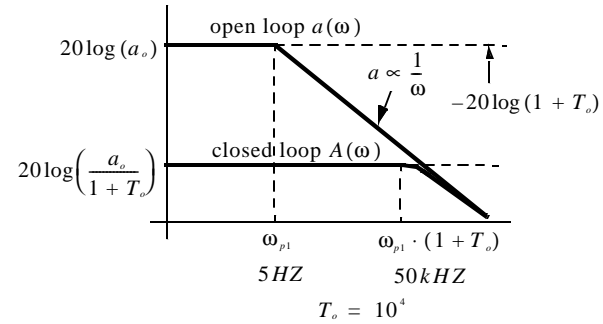
Effect of Feedback on Frequency Response (Cont.) SB-5



Gain reduction by negative feedback reduces Gain by $\left(\frac{1}{1 + T_o}\right)$ and increases bandwidth by $(1 + T_o)$

Effect of Feedback on Frequency Response (Cont.) SB-6

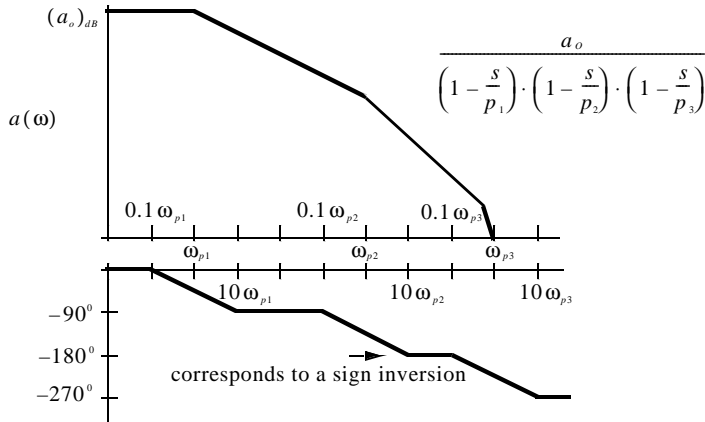
Why not let $T_o \rightarrow \infty$? Problems if we have more than one pole.



At the frequency $(10\omega_{p2})$ the phase shift is 180° or negative feedback at DC is now positive feedback.

Effect of Feedback on Frequency Response (Cont.) SB-7

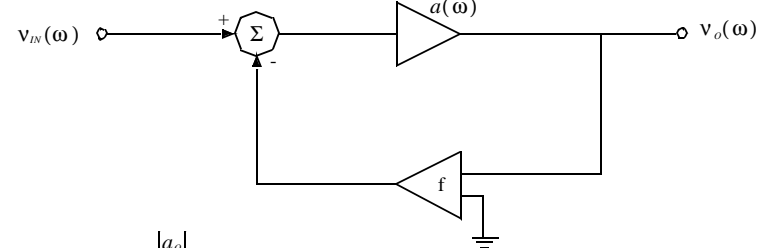Lets look at the motion of a single pole with positive feedback :




$$a(\omega) = -\frac{|a_o|}{1 - \frac{s}{p_1}} \quad p_1 = -\omega_{p1}$$

$$A(s) = \frac{a_o}{1 + T_o} \cdot \left[\frac{s}{p_1 \cdot (1 - |a_o| \cdot f)} \right]$$

Effect of Feedback on Frequency Response (Cont.) SB-8

Since,

$$T_o = -|a_o| \cdot f$$

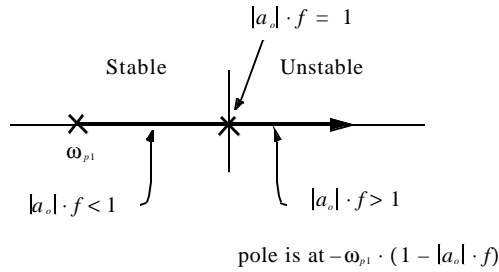

If $T < -1$ or $(1+T) < 0$ the circuit is unstable

Effect of Feedback on Frequency Response (Cont.) SB-9

The condition for stability of a multipole response is the Nyquist Criteria.

$$A(s) = \frac{a(s)}{1 + a(s) \cdot f} = \frac{a(s)}{1 + T(s)}$$

Simple Version :

If $|T(j\omega)| > 1$ at the frequency where the phase of $T(j\omega) = -180^\circ$, then the circuit is unstable.


$$T(j\omega) = T(s) \Big|_{s=j\omega}$$

$$\theta_{T(j\omega)} = \arctan \left[\frac{\text{Im}\{T(j\omega)\}}{\text{Re}\{T(j\omega)\}} \right]$$


Effect of Feedback on Frequency Response (Cont.) SB-10

Complex Nyquist Criteria :

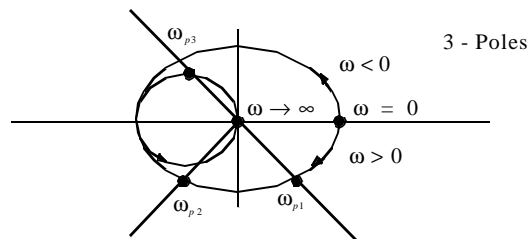
Plot $T(j\omega)$ on complex plane. As ω increases count number of times -1 is circled - even number means unstable (I Think).



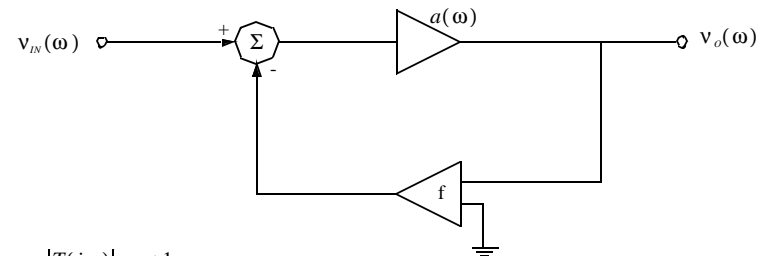Effect of Feedback on Frequency Response (Cont.) SB-11




$$|T(j\omega)|_{180^\circ} < 1$$

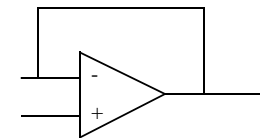

Worst Case Stability Condition

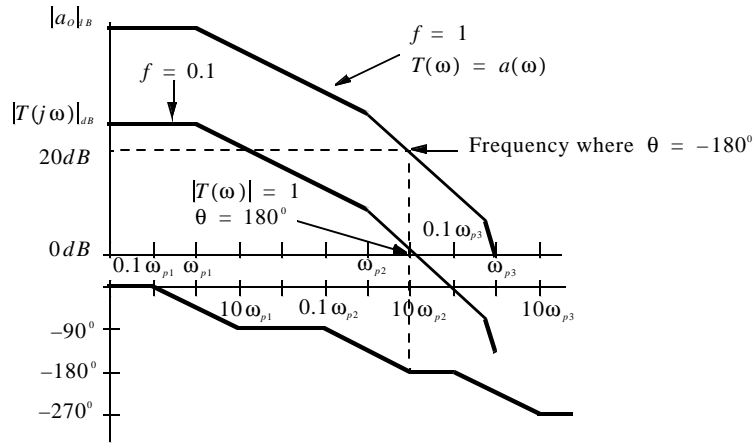Effect of Feedback on Frequency Response (Cont.) SB-12



Effect of Feedback on Frequency Response (Cont.) SB-13

PHASE MARGIN : Difference between the actual phase shift and -180°

when $|T(\omega)| = 1$


i.e. $\theta_m \equiv \text{Phase Margin} = \theta[T(\omega)] - (-180^\circ)$

if $\theta_m > 0$ then the amplifier is stable - typically $45^\circ - 60^\circ$

$$A = \frac{1}{f} \text{ more gain more stable}$$


$$R_{out} = \frac{R_o}{1 + T} \text{ higher } R_{out} \text{ with more gain}$$

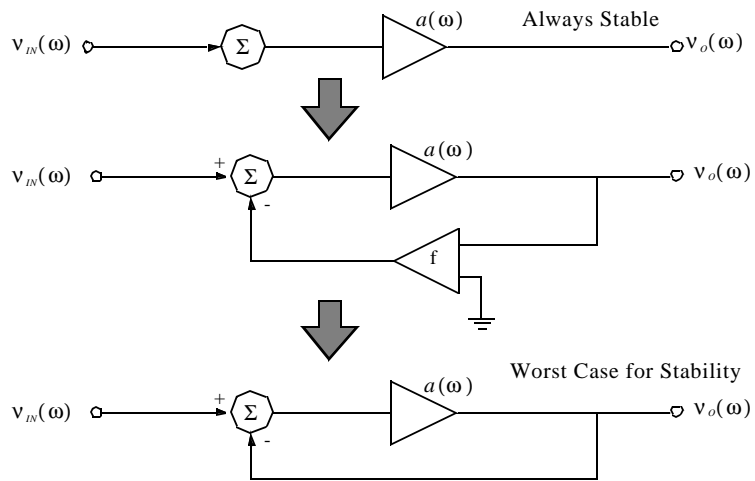Effect of Feedback on Frequency Response (Cont.) SB-14



Effect of Feedback on Frequency Response (Cont.) SB-15

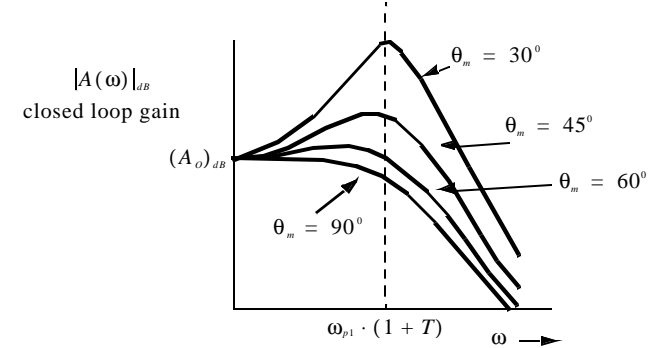As θ_m approaches 0 the amplifier is becoming unstable.



Effect of Feedback on Frequency Response (Cont.) SB-16

$$A(\omega) = \frac{a(\omega)}{1 + a(\omega) \cdot f}$$

$$a(s) = \frac{N(s)}{D(s)}$$

$$A(s) = \frac{\frac{N(s)}{D(s)}}{1 + \frac{N(s)}{D(s)} \cdot f} = \frac{N(s)}{D(s) + N(s) \cdot f}$$

← zeros of a(s)
↑ poles of a(s)


if the feedback factor is frequency dependent, then,

$$f(s) = \frac{N_f(s)}{D_f(s)}$$

$$A(s) = \frac{N(s)D(s)}{D(s)D_f(s) + N(s)N_f(s)}$$

Narrowbanding for Compensation SB-18

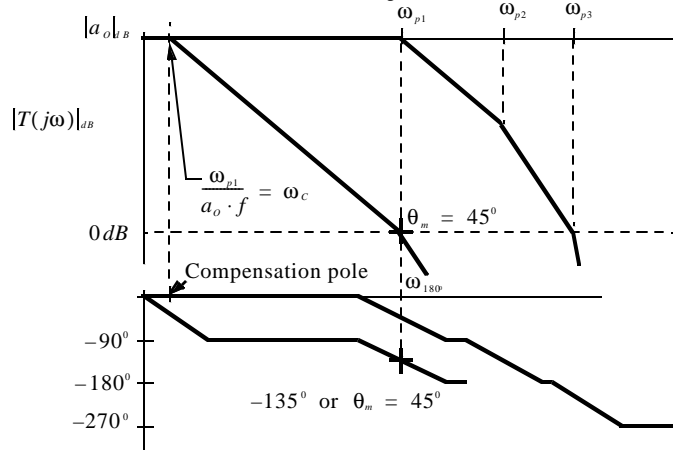This entails the addition of a dominant pole



Compensation SB-17

Compensation is the method in which an amplifier is modified so that it is stable.

One way is to decrease f (less feedback).

If ω_{180} is the frequency where,

$$\theta(a(\omega_{180})) = -180^\circ$$

then if,

$$f < \left| \frac{1}{a(\omega_{180})} \right|$$

then,

$$|T(\omega_{180})| = f \cdot |a(\omega_{180})|$$

and stability is ensured.

Narrowbanding for Compensation (Cont.) SB-19

For,

$$\theta_m = 45^\circ$$

add a compensation pole, ω_c at the frequency,

$$\frac{\omega_{p1}}{|a_{\infty}f|} = \omega_c$$

$$\omega_p = 1MHz$$

$$|a_{\infty}f| = 10^4$$

$$\omega_c = 100Hz$$


-90° of phase shift from the new compensation pole.

-45° from the second pole.

Pole Splitting



SB-20

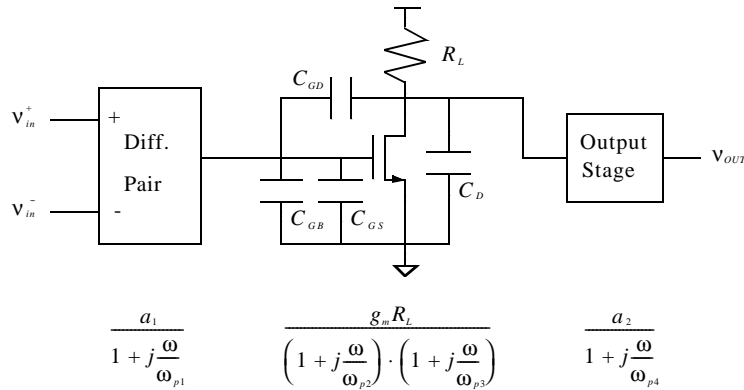It is better to use an existing pole rather than add another.



SB-22

$|A(\omega)|_{dB}$
closed loop gain

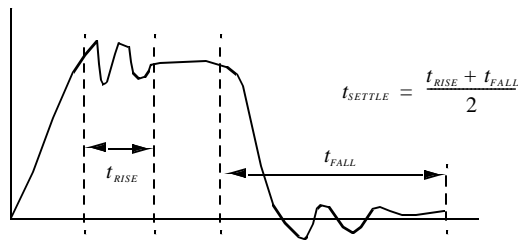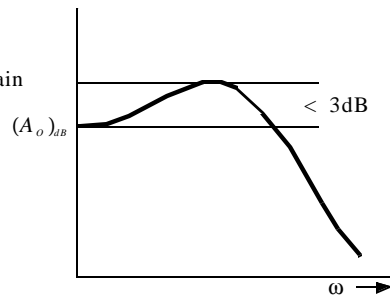

Pole Splitting (Cont.)

SB-21

Lets say ω_{p1} and ω_{p4} are given with,

$$\omega_{p4} \gg \omega_{p1}$$


$$C_{GD} \ll C_{GS}, C_D$$

then,

$$\omega_{p2} = \frac{1}{R_{DIFF} C_{GS}}$$

$$\omega_{p3} = \frac{1}{R_L C_D}$$

$$\omega_z = \frac{g_m}{C_{GD}}$$

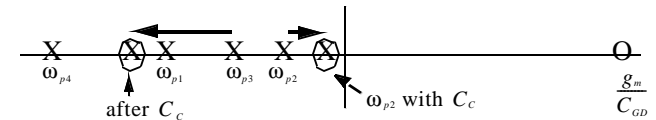

Pole Splitting (Cont.)

SB-23

If we add a compensation capacitor, C_c in parallel with C_{GD} :

$$\omega_{p2} = \frac{1}{R_{DIFF} \cdot (1 + g_m \cdot R_L) \cdot C_c}$$

$$\omega_{p3} = \frac{g_m}{C_{GS} + C_D}$$

Lets put numbers in :

$$R_{DIFF} = 10 \text{ Meg} \Omega$$

$$\omega_{p1} = 10 \cdot 10^6 \frac{\text{rad}}{\text{sec}}$$

$$R_L = 5 \text{ Meg} \Omega$$

$$\omega_{p4} = 100 \cdot 10^6 \frac{\text{rad}}{\text{sec}}$$

$$C_{GS} = 0.1 \text{ pF}$$

$$a_1 = 10^3$$

$$C_D = 0.1 \text{ pF}$$

$$a_2 = 1$$

$$g_m = 10^{-3} \text{ Mhos}$$

Pole Splitting (Cont.)

SB-24

Before compensation, and with,

$$C_{GD} = 0$$


$$\omega_{p2} = \frac{1}{10^7 \cdot 10^{-13}} = 10^6 \frac{rad}{sec}$$

$$\omega_{p3} = \frac{1}{5 \cdot 10^6 \cdot 10^{-13}} = 2 \cdot 10^6 \frac{rad}{sec}$$

$$a(\omega) = \left(\frac{10^3}{1 + j \frac{\omega}{4 \cdot 10^6}} \right) \cdot \left(\frac{10^{-3} \cdot 5 \cdot 10^6}{\left(1 + j \frac{\omega}{10^6}\right) \cdot \left(1 + j \frac{\omega}{2 \cdot 10^6}\right)} \right) \cdot \left(\frac{1}{1 + j \frac{\omega}{10^8}} \right)$$

Pole Splitting (Cont.)

SB-26

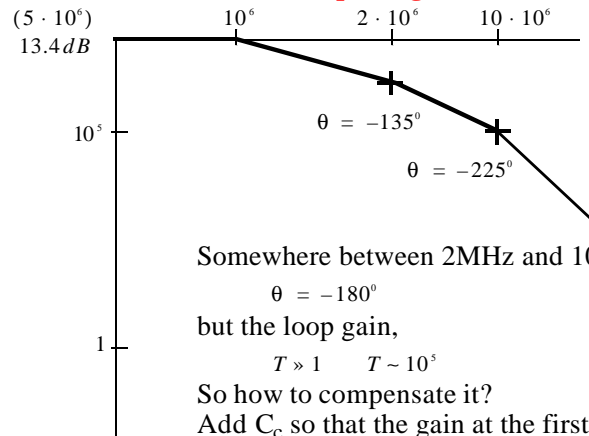

Somewhere between 2MHz and 10MHz,

$$\theta = -180^\circ$$

but the loop gain,

$$T \gg 1 \quad T \sim 10^5$$

So how to compensate it?

Add C_c so that the gain at the first non-dominant pole (ω_{p1}). since ω_{p3} will move to a higher frequency and ω_{p2} will move lower

Pole Splitting (Cont.)


SB-25

Compensate this amplifier for the worst case,

$$f = 1$$

with,

$$\theta_m = 45^\circ$$

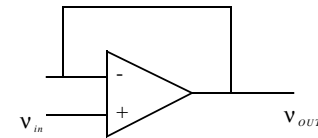

Worst Case Stability Condition

Pole Splitting (Cont.)

SB-27

$$\omega_{p2} = \frac{\omega_{p1}}{5 \times 10^6} = \frac{10^7}{5 \times 10^6} = 2 \cdot \frac{rad}{sec}$$

Formula for ω_{p2} & ω_{p3} with C_c :

$$C_c \gg C_{GS}, C_D$$

$$\omega_{p2} = \frac{1}{R_{DIFF} \cdot (1 + g_m \cdot R_L) \cdot C_c}$$

$$\omega_{p3} = \frac{g_m}{C_{GS} + C_D}$$

$$\omega_z = \frac{g_m}{C_c}$$

Pole Splitting (Cont.)

SB-28

$$C_c = 10pF$$



$$\omega_{p2} = \frac{1}{10^7 \times 5 \times 10^3 \times C_c}$$

$$\omega_{p3} = \frac{10^{-3}}{0.2 \times 10^{-12}} = 5 \times 10^9 \cdot rad/sec = 5000Mrad/sec$$


$$\omega_z = \frac{10^{-3}}{10^{-11}} = 10^8 \cdot \frac{rad}{sec}$$

So by adding a 10pF capacitor this circuit is made stable.

SB-29

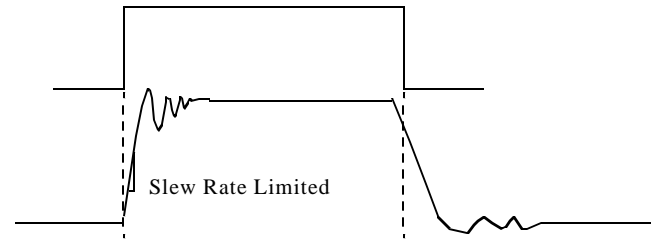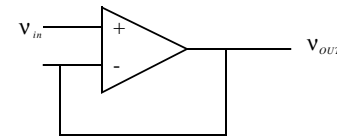


SB-30

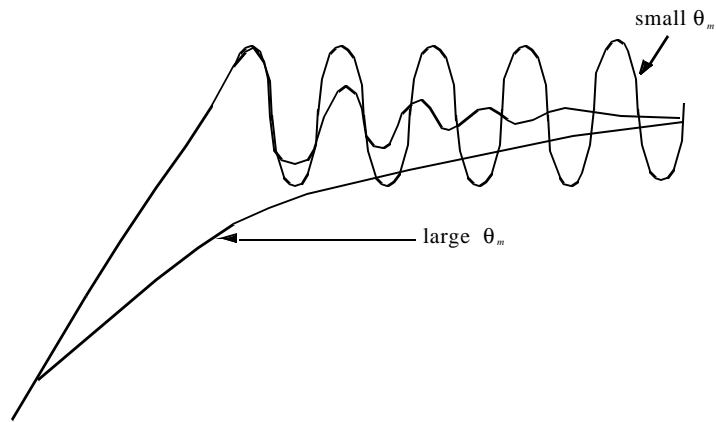


SB-31

Slew Rate & Compensation Miller Op Amp

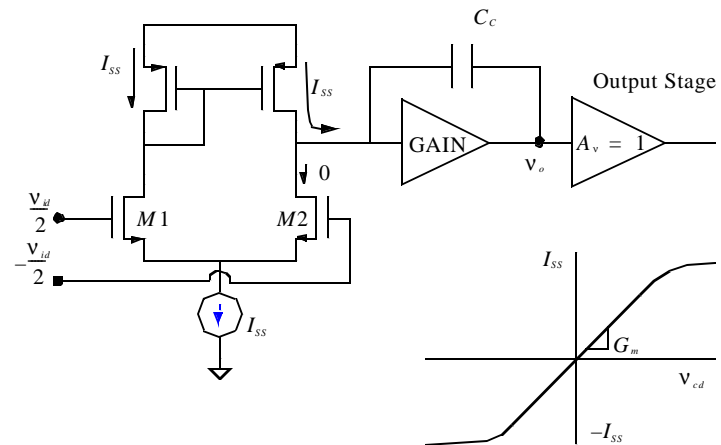


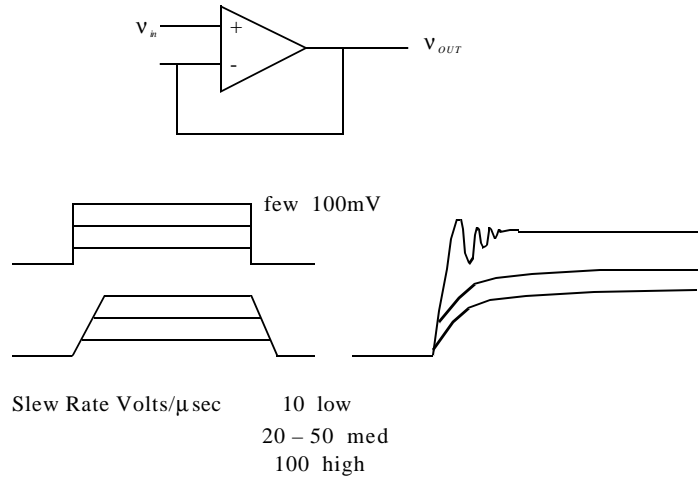Slew Rate & Compensation Miller Op Amp (Cont.) SB-32



Slew Rate & Compensation Miller Op Amp (Cont.) SB-33


Circuit situation with large v_{id}

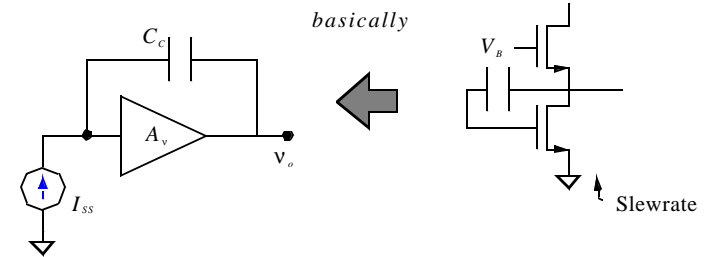

$$I_{SS} = -C_c \cdot \frac{dv_o}{dt} \quad \text{or} \quad \frac{dv_o}{dt} = -\frac{I_{SS}}{C_c} = \text{slew rate}$$

$$v_o = \frac{1}{C} \cdot \int I_{SS} \cdot dt = \frac{I_{SS}}{C} \cdot t \quad \leftarrow \text{linear with time}$$

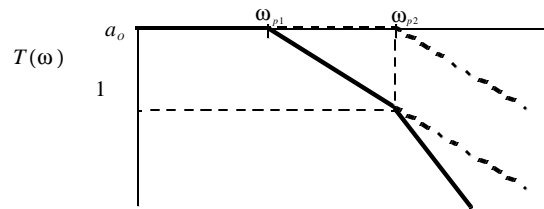Slew Rate & Compensation Miller Op Amp (Cont.) SB-34



$$\theta_m = 45^\circ$$


$$f = 1$$

$$a_o = a_{DIFF} \cdot a_g$$

Location of compensation pole :

$$\omega_c = \frac{\omega_{p2}}{a_o}$$

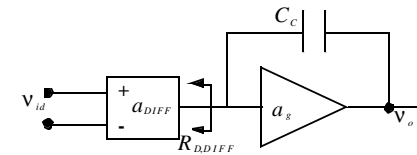Slew Rate & Compensation Miller Op Amp (Cont.) SB-35



$$a_{DIFF} = g_m \cdot R_{DDIFF}$$

$$\omega_c = \frac{1}{R_{DIFF} \cdot a_g \cdot C_c} = \frac{\omega_{p2}}{a_o} = \frac{\omega_{p2}}{a_{DIFF} \cdot a_g}$$

$$\frac{\omega_{p2}}{a_{DIFF}} = \frac{1}{R_{DDIFF} \cdot C_c} = \frac{\omega_{p2}}{g_m \cdot R_{DDIFF}}$$

$$C_c = \frac{g_m}{\omega_{p2}} \quad \text{The size of the compensation depends only on } g_m \text{ \& } \omega_{p2}$$

Slew Rate & Compensation Miller Op Amp (Cont.) SB-36

$$g_m = \frac{2 \cdot I_{DS}}{V_{DSAT}}$$

$$V_{DSAT} = \frac{2 \cdot I_{DS}}{g_m}$$

$$g_{m1} \Big|_{I_{DS} = \frac{I_{SS}}{2}}$$

$$\frac{dv_o}{dt} = \frac{I_{SS}}{C_c} = \frac{I_{SS}}{g_{m1}} \cdot \omega_{P2} = \frac{I_{SS}}{2} \cdot \frac{2}{g_{m1}} \cdot \omega_{P2}$$

$$\text{Slewwrate} = \frac{dv_o}{dt} = V_{DSAT1} \cdot \omega_{P2}$$

$$V_{DSAT} = 0.1V$$


$$\omega_{P2} = 10MHz \cdot 2\pi \quad SR = 6.3V/\mu\text{sec}$$

Slew Rate & Compensation Miller Op Amp (Cont.) SB-37


How to increase slew rate :

Increase $V_{DSAT1} \Rightarrow$ More current, smaller $\frac{W}{L}$

Increase ω_{P2}

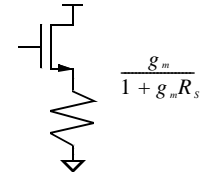

Slew rate limits max change :

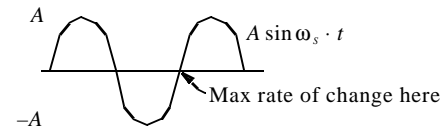



$$A = 2V \quad \omega_s = 10^6 \cdot 2\pi$$

$$SR = 13V/\mu\text{sec}$$

$$\frac{dV_{SIG}}{dt} = \omega_s \cdot A \cos \omega_s \cdot t$$

Max Value $\omega_s \cdot A$

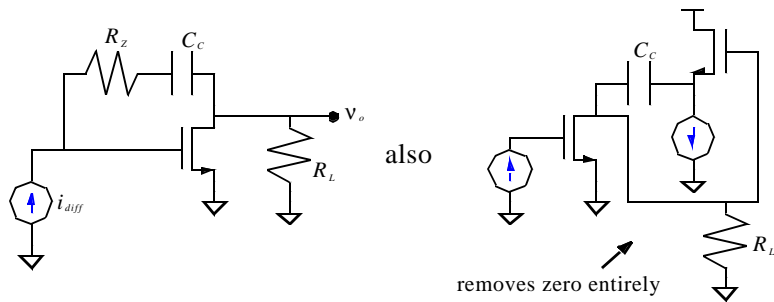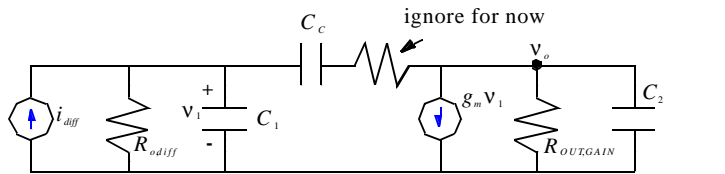MOS Miller Amp - Right Half Plane Zero SB-38



MOS Miller Amp - Right Half Plane Zero (Cont.) SB-39

$$\omega_z = \frac{1}{C_c \cdot \left(\frac{1}{g_m} - R_z \right)}$$

